	University of Ruhuna Faculty of Engineering	EE 6303 Electrical Machines II	
Dep. of Electrical and Information Engineering		Assignment 1: Three phase transformers	
		Deadline	11.07.2023

Submit a soft copy of your answer sheet via the submission link given in LMS.

- 1) An ideal 3-phase step-down transformer connected delta/star delivers power to a balanced 3-phase load of 120 kVA at 0.8 power factor. The input line voltage is 11 kV and the turn-ratio of the transformer, phase-to-phase is 10. Determine the line voltages, line currents, phase voltages and phase currents on both the primary and the secondary sides.
- 2) Two single-phase transformers operate in parallel to supply a load of $44 + j 18.6 \Omega$. The transformer A has a secondary emf of 600 V on open circuit with an internal impedance of $1.8 + j 5.6 \Omega$ referred to the secondary. The corresponding figures for transformer B are 610 V and $1.8 + j 7.4 \Omega$. Calculate the terminal voltage, current and power factor of each transformer.
- 3) A 400/100 V, 10 kVA, 2-winding transformer is to be employed as an autotransformer to supply a 400 V circuit from a 500 V source. When tested as a 2-winding transformer at rated load, 0.85 pf lagging, its efficiency is 97%.
 - a) Determine its kVA rating as an autotransformer.
 - b) Find its efficiency as an autotransformer.
- 4) A 6000 V/150 V, 50 Hz potential transformer has the following parameters with reference to Figure Q4 as seen from HV side.

$X_1 = 876 \Omega$	$X'_2 = 996 \Omega$	$X_m = 398 \text{ k}\Omega$
$R_1 = 684 \Omega$	$R'_2 = 887 \Omega$	

 - a) The primary is excited at 6400 V and the secondary is left open. Calculate the secondary voltage magnitude and phase.
 - b) The secondary is loaded with 10 k Ω resistance, repeat part a).
 - c) Calculate the percentage error in the measurement for the two cases in part a) and b).

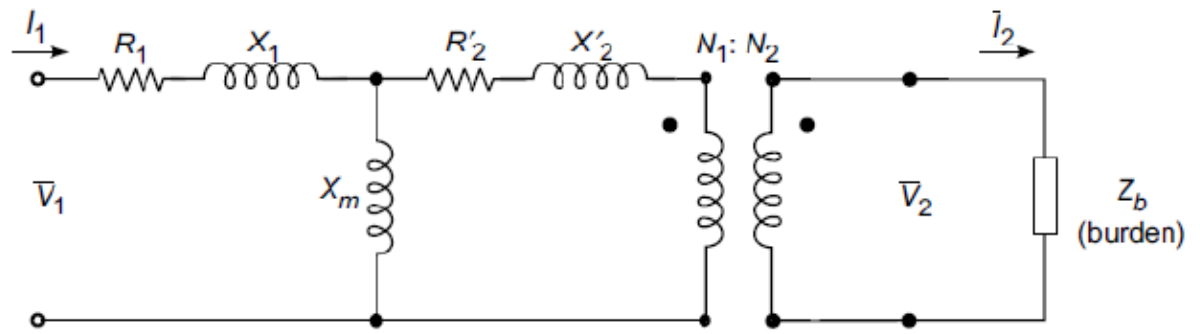


Figure Q4. Equivalent circuit of a potential transformer.